

Homework

1. Approximate the solution to the initial value problem

$$\begin{cases} x' = f(t, x) = -2x + te^{-t} \\ x(1) = 3. \end{cases}$$


in the interval $[1, 1.2]$ in 5 discrete points including the initial point. Sketch the solution. Do not use computer programs.

2. Consider the RC -circuit shown. Instead of piecewise linear functions, assume the nonlinear VI -characteristics is given by

$$V = f(I) = 3(I^3 - 2I^2 + I).$$

Assume the following parameter values for the circuit

$$C = 0.1, \quad E = 0.2.$$

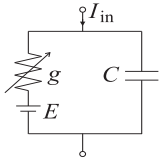

For numerical approximation and simulation, convert the circuit equations to the following system of differential equations

$$\begin{cases} V_C' = -(I_g + I_{in})/C \\ I_g' = F(V_C + E, I_g)/\epsilon \end{cases}$$

where $F(V, I) = V - f(I) = V - 3(I^3 - 2I^2 + I)$ and use $\epsilon = 0.001$. Modify appropriate `m.files` from the LectureNotes folder `matlab/mfilechcircuits/Scircuit` to do the following.

1. For $I_{in} = -0.6$, sketch the graphs of both V_C -nullcline and I_g -nullcline in the $V_C I_g$ phase plane.
2. For $I_{in} = -0.6$, use the **Matlab** solver `ode15s` to approximate the solution starting at the resting potential point $(-E, 0)$ for a time duration from $t = 0$ to $t = T = 1$. Plot both time series of the solution curves over the time interval $[0, T]$.
3. Plot the solution curve (i.e. parameterized curve $(V_C(t), I_g(t))$ from (2) in the same phase plane of (1).
4. Repeat the same tasks for parameter value $I_{in} = -0.1$. Comment on differences between the two cases.
5. $I_{in,0}$ is an oscillation **threshold** if the circuit dynamics is oscillatory for parameter values of I_{in} immediately on one side of $I_{in,0}$ but not the other side. How many thresholds for this circuit and what are they?
6. A square-burster circuit was constructed in the LectureNotes folder `matlab/mfilechcircuits/SquareBursterCircuit/PiecewiseLinearIV`. Use the mfile `SBsimulation1.m` to find an L value so that the circuit produces bursts of 6 spikes. Submit all figures from the simulation.